

CS2100 (AY2018/9 Semester 2)
Assignment #2

/15

Name: Daniel Alfred Widjaja

Tutorial Grp: 20

You are to do this assignment **on your own**. (Students found copying will be penalised.) Please fill in your **name** and **tutorial group number** in the boxes above, and your answers in the space indicated below. You are not required to show workings.

Please submit this assignment by **22 March 2019, Friday, 23:59** to the submission File on LumiNUS according to your tutorial group. Please submit either a .docx or .pdf file. Please include your name in your filename, eg: AaronTan_assign2.pdf.

Late submission and email submission will not be accepted.


1. Given a Boolean function with 8 variables A, B, C, D, E, F, G and H , what is

(a) minterm **m_{160}** ? (b) maxterm **M_{51}** ? [2 marks]

(a) $m_{160} = A \cdot B' \cdot C \cdot D' \cdot E' \cdot F' \cdot G' \cdot H'$

(b) $M_{51} = A + B + C' + D' + E + F + G' + H'$

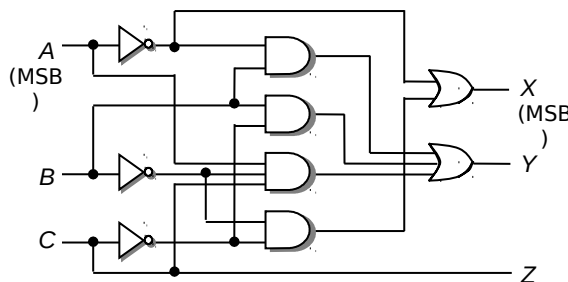2. The logic circuit below is a code converter. [4 marks]



Write out the simplified SOP expressions for X , Y and Z .

Answers: $X = A' + B' \cdot C'$

$$Y = A' \cdot B + B \cdot C' + A \cdot B' \cdot C$$

$$Z = C$$

Which of the following statement is correct about the circuit?

- A. It converts a 3-bit 2's complement number to 3-bit excess 4 code.
- B. It converts a 3-bit excess 4 code to 3-bit 2's complement number.
- C. It converts a 3-bit 2's complement number to 3-bit 1's complement number.
- D. It converts a 3-bit sign-and-magnitude code to 3-bit excess 4 code.

E. It converts a 3-bit excess 4 code to 3-bit sign-and-magnitude code.

Answer: D

3. Fill in the K-map for the function $F1(P,Q,R,S)$ below. You are not to change the layout of the given K-map. The D 's denote the don't-cares.

$$F1(P,Q,R,S) = \prod M(0, 2, 9, 10, 11, 13, 14, 15) \cdot \prod D(1, 3, 4, 7, 8) \quad [2 \text{ marks}]$$

		RS			
		00	01	11	10
PQ	00	0	X	X	0
	01	X	1	X	1
	11	1	0	0	0
	10	X	0	0	0

4. Given $F2(A,B,C,D)$ below, determine the number of prime implicants (PIs) and essential prime implicants (EPIs) on the K-map of $F2$, the simplified SOP expression and the simplified POS expression for $F2$ (where there are two or more simplified SOP/POS expressions, you need supply only one). The X's denote the don't-cares.

$$F2(A,B,C,D) = \sum m(2, 5, 8, 10, 12, 15) + \sum x(0, 6, 13, 14) \quad [4 \text{ marks}]$$

Number of PIs = 5

Number of EPIs = 2

Simplified SOP expression for $F2 = A \cdot B + B' \cdot D' + B \cdot C' \cdot D$

Simplified POS expression for $F2 = (A + B' + D) \cdot (A + B' + C') \cdot (B + D')$

- 5 Given the following function:

$$F3(A,B,C,D) = \sum m(1, 2, 4, 11, 13, 14) + \sum x(5 - 10) \quad [3 \text{ marks}]$$

- (a) Write the simplified SOP expression for $F3$.

$$F3 = A' \cdot B + A \cdot B' + C \cdot D' + C' \cdot D$$

- (b) Provide an alternative expression for $F3$ which can be implemented with at most three logic gates.

$$F3 = A \oplus B + C \oplus D$$